RF-SoP using differential ports for WLAN

Microwave Circuit and System-on-Package Lab. Graduate Inst. of Electronics Engineering, National Taiwan University

RF-SoP approaches

- Replace discrete components with embedded ones for size and area reduction.
- Addition of more functional blocks, such as an antenna or filters to the module.
- Optimize performance by replacing on-chip passives with high-Q passives embedded in package.

LTCC

- LTCC: low temperature cofire ceramic
 - Multi-layer, vias, blind vias, buried resistors
 - Passive elements, transmission lines can be placed inside or on surface of LTCC.
 - Active elements on surface


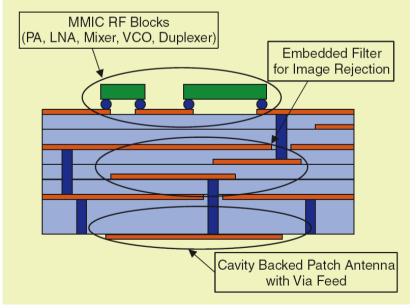


Figure 17. 3D integrated module with CBPA and embedded filter.

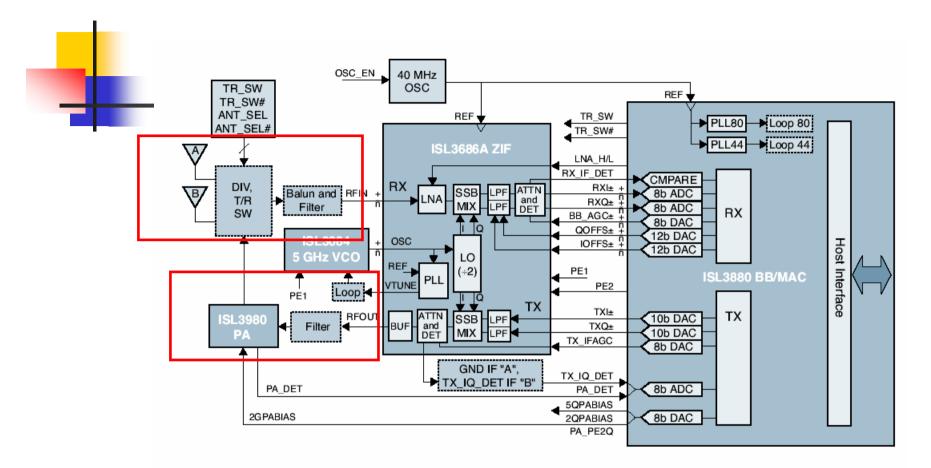



PRISM GT Block Diagram

- •Block diagram of Conexant's Prism GT chipset.
- •Balanced input or/and output at chipset.
- •We will work on components inside the red boxes by using differential transmission lines


Why use balanced circuit?

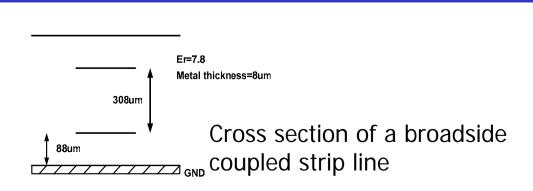- Eliminate baluns
- The differential operation could suppress the common mode interference.
- The virtual ground terminal would be compatible with the poor grounding of compact circuit.
- Antennas can also has differential feed.
- Broadside coupled stripline or microstrip line are chosen for same area occupation as single ended circuits.



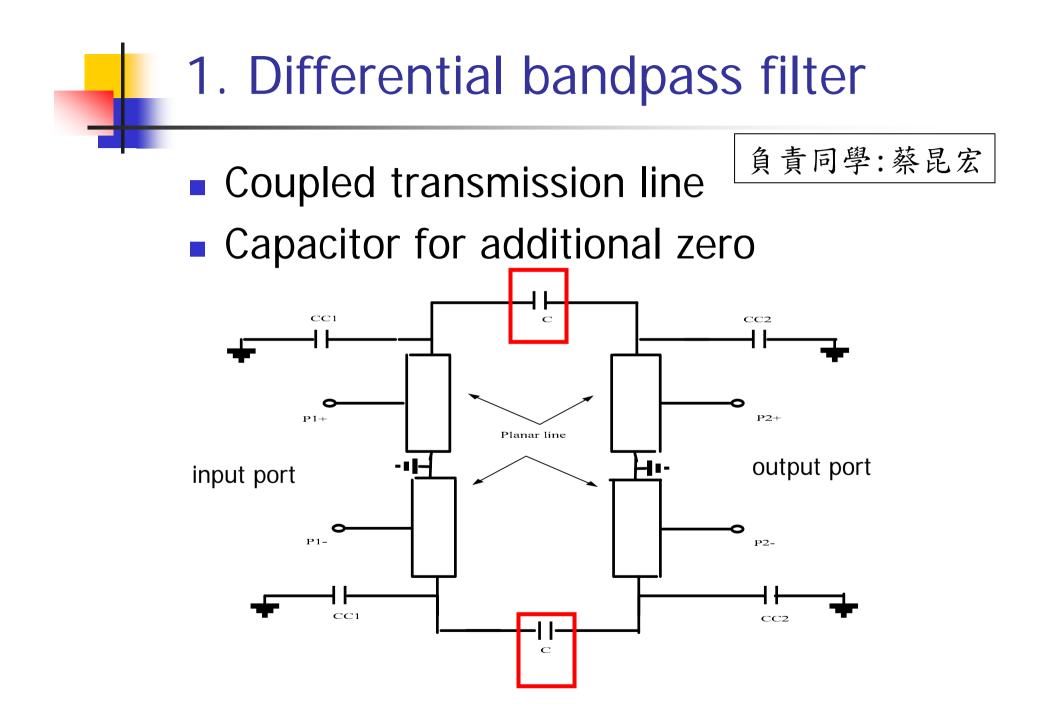

3D layout and simulation results

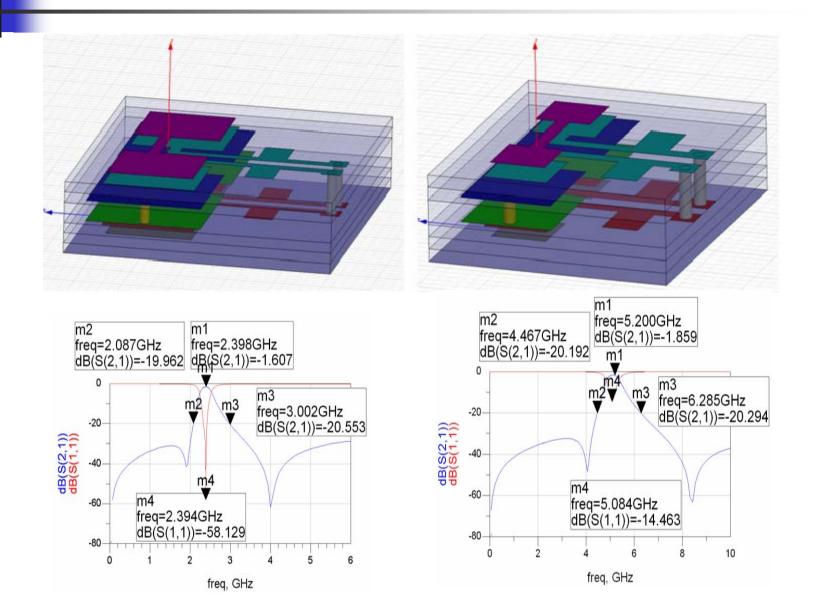


Performance comparison

	S11	S21	Attenuation of - 20dB
BPF@2.4GHz	-28dB	-1.3dB	1.9GHz [,] 3GHz
BPF+CAP.@2.4 GHz	-58dB	-1.6dB	2.1GHz [,] 3GHz
BPF@2.4GHz at [1]	-33dB	-2.2dB	2GHz [,] 3GHz
BPF@5.2GHz	-29dB	-1.1dB	4GHz [,] 6.2GHz
BPF+CAP.@5.2 GHz	-14dB	-1.8dB	4.46GHz, 6.2GHz
BPF@5.8GHz at [1]	-13dB	-2.5dB	4.8GHz [,] 6.8GHz


 [1] Young-Joon Ko, Jae Yeong Park, Jin-Hyung Ryu, Kyeong-Hak Lee, and Jong Uk Bu, "A miniaturized LTCC multi-layered front-end module for dual band WLAN(802.11a/b/g) applications," *IEEE MTT-S Diggest*, pp.536-566, June 2004.

2. Differential T/R Switch

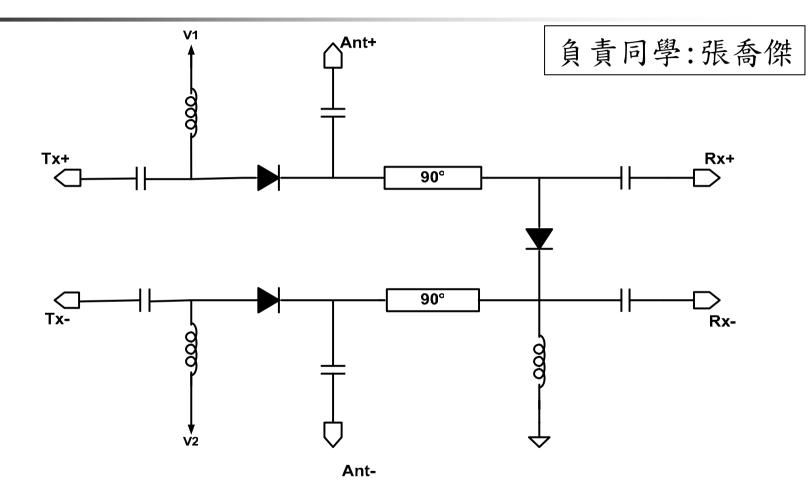

Three PIN DiodesNo DC Power consumption at Receiving Mode

LTCC Layout @2.45GHz and 5.2GHz

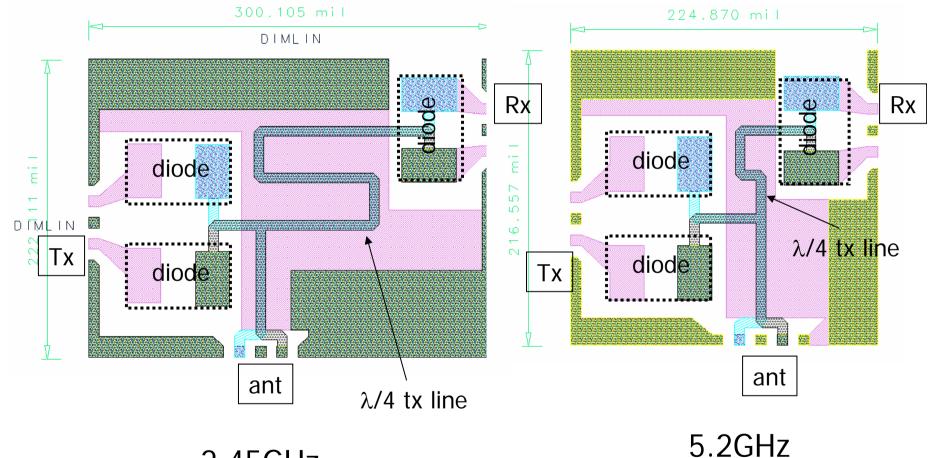

2.45GHz


802.11 a/g Simulation Data

802.11g	Mode		
Parameter	RX(0V)	TX(3mA)	
Insertion Loss@2.45GHz	0.5dB	1.84dB	
Isolation TX/RX	45.9dB	45.9dB	
Isolation ANT/RX		30.16dB	
Isolation TX/ANT	46.2dB-		
Power Handling	23dBm	23dBm	


802.11a	Mode		
Parameter	RX(0V)	TX(3mA)	
Insertion Loss@5.25GHz	2.5dB	1.836dB	
Isolation TX/RX	45dB	18.5dB	
Isolation ANT/RX		17.6dB	
Isolation TX/ANT	42dB		
Power Handling	23dBm	23dBm	

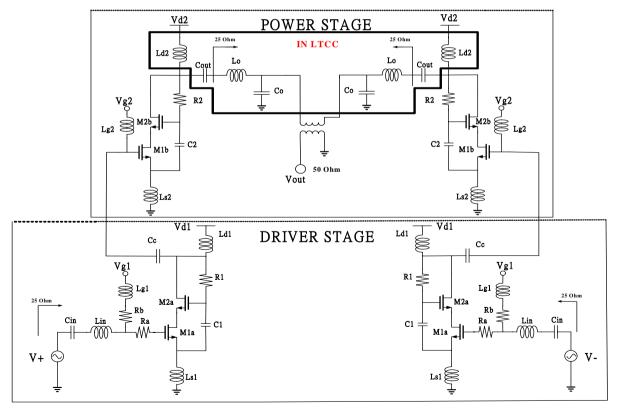3. Differential Self-biased PA for 802.11a


- Two stage differential PA, TSMC 0.18 CMOS 負責同學:黃奇順 process
- Output and input both match to 50Ω
- Driver stage is class A, power stage is class AB



Layout and simulation results

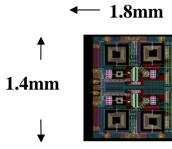

Technology	WLAN 802.11a 規格[1], [6]	TSMC 0.18um 1P6M RF_CMOS
Supply Voltage	1.8 V	1.8 V
Center Frequency	5.25GHz	5.25 GHz
Output Power (Psat)	>23 dBm	23.2 dBm
Power Added Efficiency (PAE) @ Pout = 23.2 dBm	>15 %	38 %
Output P1dB	>19 dBm	19.497 dBm
Output IP3	>26 dBm	28.8734 dBm
Power Gain @ Pin = -12.5dBm	20 dB	19.5 d B
DC current of driver stage		70.64mA
DC current of power stage		72.8mA

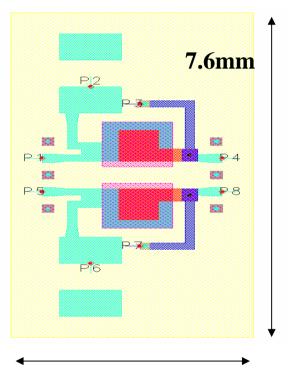

4 mm