

AAIC 2006 Homework 1

Due Fri. Mar. 17, 2006

by Tai-Cheng Lee


These problems are from "Design of Analog CMOS Integrated Circuits," by Razavi, McGraw-Hill, 2001

1. Problem 12.10

2. Problem 12.15

3. For the following sampling circuit, where $R_{on}=1k\Omega$, and $C_H =2$ pF. The circuit has been designed for a 12-bit system.

 (a) Suppose $V_{out}(t = 0) = 0$ and V_{in} is a constant, 1 V. How long does it take for the output to



reach within 0.5 LSB of V_{in} ?

(b) Now the switch is replaced by a MOS with R_{on} can be estimated as $1/\mu_n C_{ox} \frac{W}{L} (V_{gs} - V_{th})$, where $\mu_n C_{ox} W/L = 0.33mA/V^2$. Assume $V_{CK}=3$ V, $V_{th} = 0.7V$ and $v_{in}=1+\sin(\omega t)$. Write a C or MATLAB program to simulate total harmonic distortion (THD) for the input frequency from 5 MHz to 5 GHz. Note that body effect can be neglected in this problem.

(c) Now, let's neglect the RC phase shift problem in part (b). However, the finite fall time of clock (t_f) does degrade the performance. If $\omega = 100$ MHz, obtain the signal-to-distortion ratio for $t_f=100$ ps, 300 ps, 1 ns and 2 ns. For this problem, you need to derive the "actual sampling signal" and then use MATLAB FFT to obtain the answer. Verify Eq.(2.13) in the textbook.